



## Experiment #77 — Load Lines

Once past the very basic levels of transistor amplifier circuits, you'll encounter the *load line*, a graphical method of circuit design. This experiment shows you how the load line is determined and applied to circuit behavior.

### Diode Load Line

A diode is the simplest semiconductor device for which a load line can be drawn. Figure 1(A) shows a diode in series with a resistor load,  $R_L$ . For any given combination of  $V_S$  and  $R_L$ , if we know the diode's forward voltage,  $V_F$ , we can solve for the diode current,  $I_F = (V_S - V_F) / R_L$ .  $V_F$ , how-

ever, depends on  $I_F$ , so we must solve the exponential equation for  $I_F$  as a function of  $V_F$ , shown as the diode's *characteristic I-V curve* in Figure 1(B).<sup>1</sup>

Figure 1(B) also shows the less precise, but easier to use, graphical method of load lines. The load line describes what happens to voltage and current in  $R_L$ . It is drawn between the maximum and minimum possible values of current and voltage across  $R_L$ . For example, if  $I_F = 0$ , there is no voltage drop

<sup>1</sup>The Fundamental Diode Equation is presented in the "Analog Basics" chapter of any recent *ARRL Handbook*.

across the diode and the voltage across  $R_L$  is  $V_S$  — that's point A on the load line. Similarly, if  $V_F = 0$ , then  $I_F = V_S/R_L$  and that's point B on the load line.

The only point at which the load line intersects the curve is point C — the *operating point* for the circuit. The intersection is the solution of the diode's characteristic curve equation with the known value of  $R_L$  and  $V_S$ . If either  $V_S$  or  $R_L$  change, the slope or placement of the load line will change along with its intersection with the diode's characteristic curve. Let's try it!

### Operating Point Control

Build the circuit in Figure 1(A) using a 1N4001 silicon diode rectifier,  $V_S = 3$  V, and  $R_L = 1\text{ k}\Omega$ . Prepare a graph with the  $I_F$  axis showing 0 to 50 mA and the  $V_F$  axis showing 0 to 10 V. Draw the load line between point A ( $I_F = 0$  mA,  $V_F = V_S = 3$  V) and point B ( $I_F = V_S / R_L = 3$  mA,  $V_F = 0$  V).

Measure the diode's forward voltage,  $V_F$ , and use Ohm's Law to calculate  $I_F$  from the voltage across  $R_L$  or measure it directly with a meter. The values should be somewhere around 0.6 V and 2.4 mA. When that point is plotted, it should be very close to or on the load line.

Vary  $V_S$  from 1 to 10 V in steps of 1 V, calculating point A and B and drawing a new load line at each step. Measure the diode voltage and circuit current as before, plotting the combination on the graph and confirming that each point is on a load line. You will start to see the diode's characteristic curve appear as the sequence of plotted points!

Return  $V_S$  to 3 V and change  $R_L$  to each of the following values, drawing a new load line at each step: 100, 220, 470, 1000, 2.2 k, and 4.7 k $\Omega$ . Measure and plot  $V_F$  and  $I_F$  at each step. This will fill in even more points, each very close to the load line for that value of  $R_L$ . As you can see, if you had enough values of  $R_L$  and sufficient power supply range, you could determine the diode's characteristic curve exactly!

You'll also have noticed that while you were only varying  $V_S$ , the load lines were parallel, but when  $R_L$  was varied, the load line slopes changed. That's because the slope of the load line is  $-1/R_L$ . Lower load resistance results in a steeper load line.

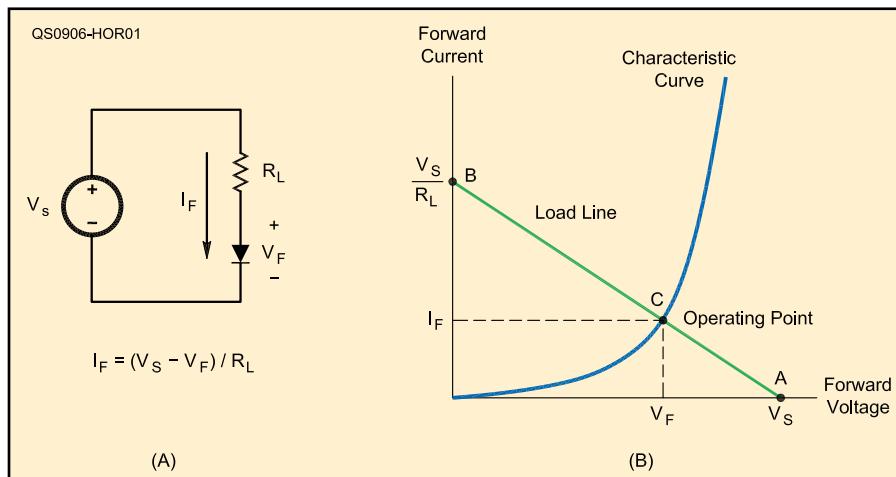


Figure 1 — The simple circuit at (A) can be used to determine the diode's characteristic curve at (B). The intersection of the load line and the characteristic curve is the circuit's operating point.

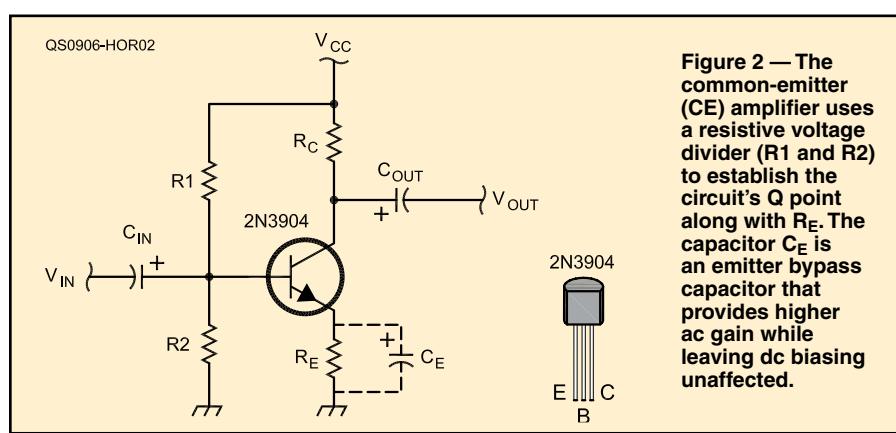


Figure 2 — The common-emitter (CE) amplifier uses a resistive voltage divider ( $R_1$  and  $R_2$ ) to establish the circuit's Q point along with  $R_E$ . The capacitor  $C_E$  is an emitter bypass capacitor that provides higher ac gain while leaving dc biasing unaffected.

## Transistor Amplifier Load Line

The load line is much more useful in designing transistor circuits, since current and voltage can take wide ranges of values. The common emitter (CE) amplifier in Figure 2, from the first Hands-On Radio experiment is one you'll use frequently, so we'll use it as an example.<sup>2</sup> This circuit uses self bias and emitter degeneration to establish a stable *Q point* (the operating point with no input signal).

The characteristic curves for a typical 2N3904 NPN transistor in the CE configuration are shown in Figure 3. Instead of just having a single characteristic curve as did the diode, a transistor's  $I_C$ – $V_{CE}$  characteristic curve can change. As base current varies, the height of the curve changes on the graph. The set of curves show "snapshots" of the transistor's characteristic curve, each at a different value of base current.

Because the load for the circuit is resistive (consisting of  $R_C + R_E$ ), the operating point falls along the dc load line drawn on the characteristic curves. We'll get to the ac load line later. As with the diode circuit, the intersection of the load line with the characteristic curve corresponding to the value of base current is the circuit's operating point. If you imagine one of the constant base current lines moving up and down as an input signal varies the base current, you can see its intersection with the load line moving, too. When no signal is applied, the base current is fixed at the level of bias current chosen by the designer and that operating point is the circuit's *Q* point. In the case of our CE amplifier, the values of  $R_1$ ,  $R_2$  and  $R_E$  determine

the location of the *Q* point by controlling the value of the base bias current.

$V_{CC}$  and the values of  $R_C$  and  $R_E$  determine the orientation of the load line. The two end points of the load line correspond to transistor saturation [ $I_{C\text{sat}} = V_{CC} / (R_C + R_E)$  on the  $I_C$  axis] and cutoff ( $V_{CC}$  on the  $V_{CE}$  axis). The slope of the load line is  $-1/(R_C + R_E)$ , because the output current of the transistor flows through both the collector and emitter resistors.

In order to experiment with the load line, here are a set of components that will result in a *Q* point of  $I_{CQ} = 4$  mA,  $V_{CEQ} = 5$  V and a voltage gain of  $-5$  with  $V_{CC} = +12$  V:  $R_E = 270 \Omega$ ,  $R_1 = 39$  k $\Omega$ ,  $R_2 = 6.8$  k $\Omega$ , and  $R_C = 1.5$  k $\Omega$ . (10  $\mu$ F capacitors will be fine for  $C_{IN}$  and  $C_{OUT}$ .) Download and print the sample 2N3904 characteristic curves from the Hands-On Radio Web site and draw the load line between cutoff and saturation in this circuit. (The *Q* point should be on the load line.)

Build the circuit and verify that the values of  $I_{CQ}$  and  $V_{CEQ}$  are about right. Apply a 1 kHz, 0.5 V<sub>p-p</sub> sine wave at the input and verify that the output signal is about five times larger and inverted from the input. Increase the input voltage until the output waveform becomes clipped at either the top or bottom and then reduce the input voltage by about half.

Now move the *Q* point by changing the value of  $I_{BQ}$ . To do this without changing the load line, adjust the ratio of  $R_1$  and  $R_2$  to change  $V_B$ , keeping the sum of the resistors in the range of 20 k to 50 k $\Omega$ . (You can substitute a 50 k $\Omega$  potentiometer for  $R_1$  and  $R_2$ , with the wiper connected to the transistor base.) Measure the new values of  $I_{CQ}$  and  $V_{CEQ}$ , locate the new *Q* point on the load line, and observe the effect on the output waveform. For example, doubling the value of  $R_2$  will raise the value of  $I_{BQ}$  dramatically

and probably cause the output waveform to be clipped at the bottom. This is because the higher bias current has moved the *Q* point farther along the load line toward saturation (left), making it easier for an input signal to drive  $V_{CE}$  lower into the saturation region.

## AC Load Lines

Figure 2 shows an *emitter bypass* capacitor,  $C_E$ , next to  $R_E$ . When  $C_E$  is connected across  $R_E$ , the circuit has a different ac voltage gain  $A_V = -R_C/r_e$  ( $r_e$  is the internal emitter resistance of a few ohms) than dc gain  $A_V = -R_C/R_E$ . For an ac signal, the circuit operates on a separate ac load line as shown in Figure 3, because  $R_E$  has been effectively short circuited for ac signals. Without  $R_E$ , the slope of the ac load line is  $-1/R_C$ , steeper than for the dc load line. The ac and dc load lines intersect at the circuit's *Q* point because the circuit's ac and dc operation is the same if the ac input signal is zero.

## Parts List<sup>3</sup>

- 1N4001 diode
- 2N3904 transistor
- 100, 220, 270, 470, 1000, 1.5 k, 2.2 k, 4.7 k, 6.8 k and 39 k $\Omega$ , 1/4 W resistors
- 3 each 10  $\mu$ F, 25 V electrolytic capacitors

## Recommended Reading

Even for non-engineers, used copies of first- and second-year circuit engineering textbooks make fine workbench references for all sorts of circuit questions. Two of my favorites are Hayt and Kemmerly's *Engineering Circuit Analysis* and Millen and Grabel's *Microelectronics*, both published by McGraw-Hill. The former is good for basic R-L-C circuit mechanics and the latter for semiconductor circuits.

## Next Month

You've heard terms before such as "SWR bridge," "noise bridge," "Wheatstone bridge" and so forth. We'll cross that bridge next month as we take a look at bridge circuits and why they are so useful.

<sup>3</sup>A parts kit for the first 61 experiments is available from your ARRL dealer or the ARRL Bookstore, ARRL order no. 1255K. Telephone 860-594-0355, or toll-free in the US 888-277-5289; [www.arrl.org/shop/pubsales@arrl.org](http://www.arrl.org/shop/pubsales@arrl.org).



## Strays

### I would like to get in touch with...

◊ any Amateur Radio ops who are employed by Munich Reinsurance America Inc. — *Mike Haydon, AC2Q, 1420 Fairway, Rantoul, IL 61866, tel 217-892-1658*

<sup>2</sup>Previous Hands-On Radio columns and a complete parts list for all experiments are available to ARRL members at [www.arrl.org/tis/info/HTML/Hands-On-Radio](http://www.arrl.org/tis/info/HTML/Hands-On-Radio) and in Experiment #76 (see next note).

