



## ARRL Periodicals Archive – Search Results

### A membership benefit of ARRL and the ARRL Technical Information Service

**ARRL Members:** You may print a copy for personal use. Any other use of the information requires permission (see Copyright/Reprint Notice below).

**Need a higher quality reprint or scan?** Some of the scans contained within the periodical archive were produced with older imaging technology. If you require a higher quality reprint or scan, please contact the ARRL Technical Information Service for assistance. Photocopies are \$3 for ARRL members, \$5 for nonmembers. For members, TIS can send the photocopies immediately and include an invoice. Nonmembers must prepay. Details are available at [www.arrl.org/tis](http://www.arrl.org/tis) or email [photocopy@arrl.org](mailto:photocopy@arrl.org).

**QST on CD-ROM:** Annual CD-ROMs are available for recent publication years. For details and ordering information, visit [www.arrl.org/qst](http://www.arrl.org/qst).

**Non-Members:** Get access to the ARRL Periodicals Archive when you join ARRL today at [www.arrl.org/join](http://www.arrl.org/join). For a complete list of membership benefits, visit [www.arrl.org/benefits](http://www.arrl.org/benefits).

#### Copyright/Reprint Notice

In general, all ARRL content is copyrighted. ARRL articles, pages, or documents--printed and online--are not in the public domain. Therefore, they may not be freely distributed or copied. Additionally, no part of this document may be copied, sold to third parties, or otherwise commercially exploited without the explicit prior written consent of ARRL. You cannot post this document to a Web site or otherwise distribute it to others through any electronic medium.


For permission to quote or reprint material from ARRL, send a request including the issue date, a description of the material requested, and a description of where you intend to use the reprinted material to the ARRL Editorial & Production Department: [permission@arrl.org](mailto:permission@arrl.org).

**QST Issue:** Jul 1954

**Title:** Multiband Tuning Circuits

**Author:** R.W. Johnson, W6MUR

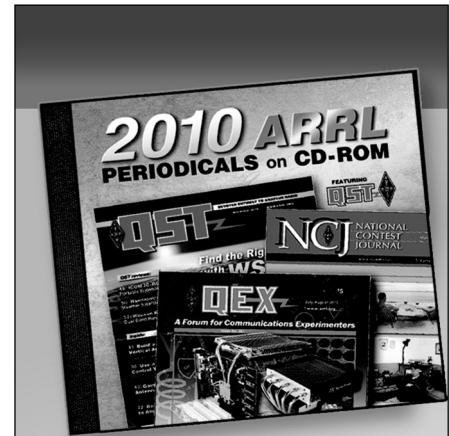[Click Here to Report a Problem with this File](#)



## 2010 ARRL Periodicals on CD-ROM

ARRL's popular journals are available on a compact, fully-searchable CD-ROM. Every word and photo published throughout 2010 is included!

- **QST** The official membership journal of ARRL
- **NCJ** National Contest Journal
- **QEX** Forum for Communications Experimenters

**SEARCH** the full text of every article by entering titles, call signs, names—almost any word. **SEE** every word, photo (including color images), drawing and table in technical and general-interest features, columns and product reviews, plus all advertisements. **PRINT** what you see, or copy it into other applications.

**System Requirements:** Microsoft Windows™ and Macintosh systems, using the industry standard Adobe® Acrobat® Reader® software. The Acrobat Reader is a free download at [www.adobe.com](http://www.adobe.com).

#### 2010 ARRL Periodicals on CD-ROM

ARRL Order No. 2001  
**Only \$24.95\***

\*plus shipping and handling

Additional sets available:

2009 Ed., ARRL Order No. 1486, \$24.95  
2008 Ed., ARRL Order No. 9406, \$24.95  
2007 Ed., ARRL Order No. 1204, \$19.95  
2006 Ed., ARRL Order No. 9841, \$19.95  
2005 Ed., ARRL Order No. 9574, \$19.95  
2004 Ed., ARRL Order No. 9396, \$19.95  
2003 Ed., ARRL Order No. 9124, \$19.95  
2002 Ed., ARRL Order No. 8802, \$19.95  
2001 Ed., ARRL Order No. 8632, \$19.95



**ARRL** The national association for AMATEUR RADIO™

SHOP DIRECT or call for a dealer near you.  
ONLINE [WWW.ARRL.ORG/SHOP](http://WWW.ARRL.ORG/SHOP)  
ORDER TOLL-FREE 888/277-5289 (US)

# Multiband Tuning Circuits

## Some Considerations in the Design of Single-Ended Networks

BY R. W. JOHNSON,\* W6MUR

\* In recent months, we have been hearing more and more about multiband tuning circuits — circuits that cover 3.5 Mc. to 30 Mc., for instance, without switching or changing coils. This article covers the design of the single-ended type, and considers some possible variations from the popular version of the circuit.

A MULTIBAND tuning circuit was introduced by King<sup>1</sup> of the National Company in 1948. The circuit has been used in a recent transmitter by Chambers,<sup>2</sup> and is commercially available as the National Company Type MB-150 and MB-40L. There appears to have been only scant design data<sup>3</sup> presented on this circuit, to permit the average amateur to design his own circuit. There also has been overlooked a possible modification of the circuit using but one tapped coil instead of the two coils usually used. In this article, both of these subjects will be discussed.

### Circuit Description

The basic circuit of King is shown in Fig. 1, in single-ended form. Equal capacitors are used

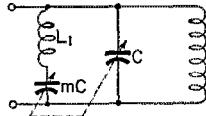


Fig. 1 — Basic circuit of a single-ended multiband tuner.

in the National circuits, but we will not restrict this discussion to equal capacitors. The capacitors are ganged together, and the coils (in the simplest case) have no mutual inductance between them. This circuit, properly designed, is capable of tuning ratios equal to the capacity ratio ( $C_{\max}/C_{\min}$ ) instead of the square root of this capacity ratio as in ordinary circuits. Thus a continuous 8:1 or 9:1 frequency range is possible with this circuit, without coil switching.

### Calibration

There are simultaneously always two parallel-resonant frequencies for the circuit of Fig. 1, as well as one series-resonant frequency. The

two parallel-resonant frequencies may or may not be harmonically related, depending on design. The series-resonant frequency always lies between the parallel-resonant frequencies, and can even be used to advantage in suppression of certain harmonics.

If  $f_0$  is defined as the resonant frequency of  $L_2C$  taken alone, then the parallel-resonant frequencies of the total circuit are

$$f_{r1} = K_1 f_0 \quad (1)$$

$$\text{and} \quad f_{r2} = K_2 f_0 \quad (2)$$

where  $K_1$  and  $K_2$  are constant for all settings of  $C$ , and depend on  $L_1$ ,  $L_2$  and  $m$  of Fig. 1. If, as  $C$  is tuned through its range,  $f_0$  changes from  $f_{o1}$  (the lowest frequency) to  $f_{o2}$  (the highest frequency), frequencies  $f_{r1}$  and  $f_{r2}$  change from  $K_1 f_{o1}$  to  $K_1 f_{o2}$ , and from  $K_2 f_{o1}$  to  $K_2 f_{o2}$ , respec-

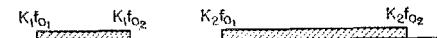


Fig. 2 — Frequency-scale representation of tuning range.

tively. This situation is depicted in Fig. 2 on a frequency scale (not tuning scale). The two bands occupy the same positions on the capacitor tuning dial even though they are separated in frequency.

Since  $K_1$  and  $K_2$  depend only on  $L_1$ ,  $L_2$  and  $m$  of Fig. 1, they can be chosen arbitrarily, within limits.  $K_1$  is a number less than unity, and  $K_2$  is a number greater than unity, for realizable cases. The ratio  $K_2/K_1$  can be almost anything desired, which means that the two bands of Fig. 2 can (a) overlap, (b) be adjacent, or (c) be separated, on the frequency scale. The maximum possible continuous (all frequencies covered) tuning range occurs in case (b), or when  $K_1 f_{o2} = K_2 f_{o1}$ , or  $K_2/K_1 = f_{o2}/f_{o1}$ . The tuning ratio for this case is  $K_2 f_{o2}/K_1 f_{o1} = (f_{o2}/f_{o1})^2 = C_{\max}/C_{\min}$ .

Selection of parameters is thus determined by the desired tuning ratios, or in other words, by  $K_2$  and  $K_1$ . The design must be such that  $K_2/K_1$  is about midway between integers, if harmonic response is to be minimized. We therefore need the relation between the  $K$ s and the circuit parameters.

### Relation for $K$

Input admittance of the circuit of Fig. 1 can be written in the usual fashion and set equal to zero. A fourth-degree quadratic frequency equation results, giving the parallel-resonant fre-

\*% The Ralph Parsons Company, Pasadena 8, Calif.

<sup>1</sup> King, "No Turrets — Just Tune!" QST, March, 1948.

<sup>2</sup> Chambers, "Three-Control Six-Band 813 Transmitter," QST, Jan., 1954.

<sup>3</sup> DiMarco, "Circuitos de Resonancia Multiple y Su Aplicacion en los transmisores para Aficionados," Revista Telefonica Electronica (Argentina), March, 1954.

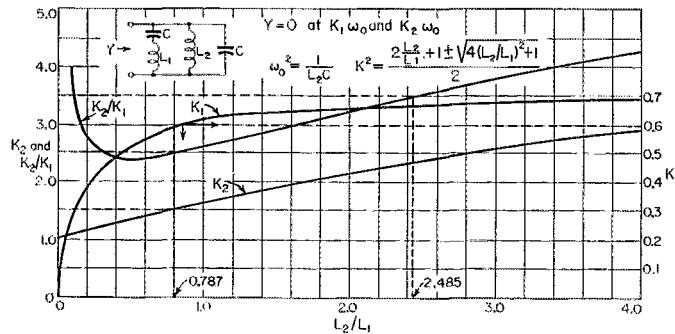


Fig. 3 — Curves of  $K_2$ ,  $K_1$ , and the ratio  $K_2/K_1$  vs.  $L_2/L_1$  for equal capacitors ( $m = 1$ ).

quencies (and hence  $K$ ) when solved. The relation for  $K$  is

$$\left. \begin{aligned} K_1^2 &= \frac{S - \sqrt{S^2 - 4 \frac{L_2}{mL_1}}}{2} = (f_{r_1}/f_0)^2 \\ K_2^2 &= \frac{S + \sqrt{S^2 - 4 \frac{L_2}{mL_1}}}{2} = (f_{r_2}/f_0)^2, \end{aligned} \right\} \quad (3)$$

where  $S = \frac{L_2(1+m)}{L_1 m} + 1$ , and  $f_0 = \frac{1}{2\pi\sqrt{L_2 C}}$

Since  $L_2/L_1$  is usually desired when given  $m$  and  $K$ , Eq. (3) can be rearranged to give this result. Thus,

$$L_2/L_1 = mK^2 \frac{K^2 - 1}{(1 + m)K^2 - 1} \quad (4)$$

which is valid for either  $K_1$  or  $K_2$ . For the usual case of equal capacitors,  $m = 1$  and Eqs. (3) and (4) become

$$K^2 = \frac{2L_2/L_1 + 1 \pm \sqrt{4(L_2/L_1)^2 + 1}}{2} \quad (3a)$$

and  $L_2/L_1 = K^2 \left( \frac{K^2 - 1}{2K^2 - 1} \right)$  (4a)

In Eq. (3a), the plus signs is used in solving for  $K_2$  and the minus sign for  $K_1$ .

Curves of  $K_2$ ,  $K_1$  and the ratio  $K_2/K_1$  vs.  $L_2/L_1$  are shown in Figs. 3 and 4. Fig. 3 is for equal capacitors ( $m = 1$ ), and Fig. 4 is for  $m = 0.5$ . Preferred operating points, to avoid harmonic responses, are shown on the curves.

If unequal but ganged capacitors are used, then  $m \neq 1$ . As can be seen from Fig. 4, the preferred operating point,  $K_2/K_1 = 2.5$ , falls at

$L_2/L_1 = 1.06$  when  $m = 0.5$ . Thus, if it is more convenient to use identical coils for  $L_1$  and  $L_2$ ,  $m$  can be chosen accordingly. The value  $m = 0.789$  gives  $L_1 = L_2$  and  $K_2/K_1 = 2.5$ .

#### Example

As a design example, suppose we desire to tune all amateur bands in the range 3.5-21.5 Mc. Assume that equal ganged capacitors are used, and that the available capacitor ratio is at least 6.25:1 (corresponding to, say, 150  $\mu\text{uf}$ . maximum and 24  $\mu\text{uf}$ . minimum). If we want continuous frequency scale coverage, we would choose  $K_2/K_1 = (6.25)^{1/2} = 2.5$ . This value is a preferred operating point in Fig. 3, at which  $L_2/L_1 = 0.8$ ,  $K_2 = 1.5$  and  $K_1 = 0.6$ . The lowest desired frequency, 3.5 Mc., is  $K_1 f_{r_1}$ , so that  $f_{r_1}$  (the resonant frequency of  $L_2 C_{\max}$ ) is  $3.5/0.6 = 5.83$  Mc. For a given capacitor, coil  $L_2$  is determined from this frequency of 5.83 Mc. Coil  $L_1 = L_2/0.8 = 1.25L_2$ . At minimum capacity, the resonant frequency of  $L_2$ ,  $C_{\min}$  is  $5.83 \times 2.5 = 14.6$  Mc. Thus, the two bands A and B of Fig. 2 extend from  $0.6 \times 5.83 = 3.5$  Mc. to  $0.6 \times 14.6 = 8.75$  Mc., and from  $1.5 \times 5.83 = 8.75$  Mc. to  $1.5 \times 14.6 = 21.9$  Mc. These two bands are of course coincident across the dial, and are covered simultaneously in 180° of capacitor rotation.

#### Coupled Impedance

Output coupling can be to coil  $L_2$  only. In this case, parallel-resonant impedance is about  $K^2$  times what it would be for a normal  $L_2 C$  circuit. This means that in the lowest band, where  $K_1 (< 1)$  is used, capacitor  $C$  can be smaller than that which would otherwise be

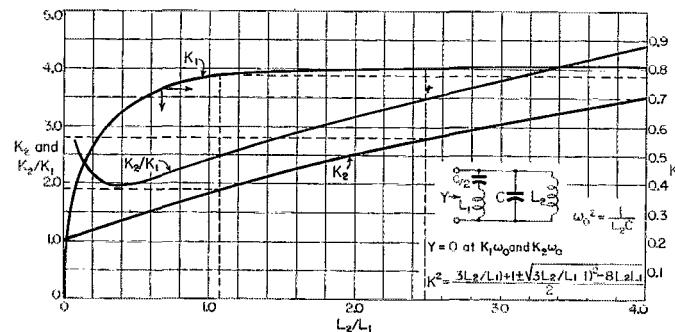


Fig. 4 — Curves of  $K_2$ ,  $K_1$ , and the ratio  $K_2/K_1$  vs.  $L_2/L_1$  for  $m = 0.5$ .

necessary; and in the higher band, where  $K_2$  ( $> 1$ ) is used,  $C$  can be larger than would otherwise be necessary.  $L/C$  ratio and ease of coupling thus tend to remain more constant with this circuit than with an ordinary resonant circuit. This was pointed out by King.<sup>1</sup>

#### Coupled Coils

The general case, where mutual inductance exists between  $L_2$  and  $L_1$ , has been worked out, but the results will not be presented here, ex-

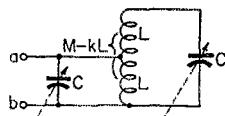


Fig. 5 — Multiband-tuner circuit using a center-tapped coil.

cept for one special case that is extremely useful. This case is that of a center-tapped coil, connected as shown in Fig. 5 with a split-stator capacitor  $C$ .


Connection to the tank circuit is made at terminals  $a$  and  $b$  in Fig. 5. The impedance

and is the resonant frequency of half the total coil taken alone with  $C$ . A curve of Eq. (5), showing  $K_1$ ,  $K_2$  and  $K_2/K_1$  vs. coupling coefficient  $k$  is shown in Fig. 6. Preferred operating points, to avoid harmonic response, are also indicated in Fig. 6.

#### Estimation of Coupling Coefficient

To use the curves of Fig. 6 or the relations of Eq. (5), a relation between coupling coefficient and coil dimensions is needed. Fortunately, this relation is not complex for a center-tapped coil. As shown in Fig. 7, a center-tapped coil can be replaced by a T equivalent. Looking into terminals  $a-b$  or  $b-c$  we see merely  $L$ , but looking into terminals  $a-c$  we see  $2L(1+k)$ . One can apply the Wheeler formula<sup>4</sup> for the inductance of a single-layer solenoid that is not too short (length at least equal to 0.8 times diameter) to solve for coupling coefficient  $k$ . This is done by first calculating the inductance between  $a-b$  (or  $b-c$ ) for a coil of half the total length and half the total turns, and then the inductance between  $a-c$  for a coil of the total length and total turns. These two relations when solved simultaneously

Fig. 6 — Curve of Eq. (4), showing  $K_1$ ,  $K_2$ , and  $K_2/K_1$  vs. coupling coefficient  $k$ .

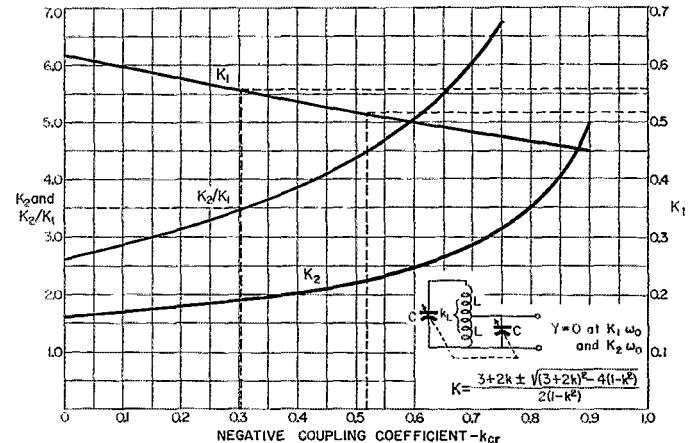

between  $a$  and  $b$  is parallel-resonant at  $K_1 f_0$  and  $K_2 f_0$  as before, where  $K$  is now given by the relations

$$K_1^2 = \frac{3+2k - \sqrt{(3+2k)^2 - 4(1-k^2)}}{2(1-k^2)}, \quad (5)$$

$$\text{and } K_2^2 = \frac{3+2k + \sqrt{(3+2k)^2 - 4(1-k^2)}}{2(1-k^2)},$$

where  $k$  is the coupling coefficient between the two halves of the coil. ( $k$  is negative for this case, but this has already been considered in Eq. (5), to avoid errors in using the relations.) Frequency  $f_0$  for use with Eq. (5) is given by

$$f_0 = \frac{1}{2\pi\sqrt{LC}},$$

<sup>4</sup> Terman, *Radio Engineer's Handbook*, 1st ed., 1943, McGraw-Hill, p. 55.

give coupling coefficient as

$$k = \frac{9}{9 + 20(l/d)} \quad (6)$$

where  $k$  is of the correct sign for substitution into Eq. (5).  $(l/d)$  is the ratio of length to diameter of the coil, in the same units of measurement. Eq. (6) holds only for values of  $(l/d)$  of about 0.8 or greater. A curve of  $k$  vs.  $(l/d)$  is shown in Fig. 8. The portion much below  $(l/d) = 0.8$  has been obtained by another more exact inductance formula, but with the same approach.

#### Example

Suppose we wish to cover the range 3.5-30 Mc., such as to tune all amateur bands. For a given capacitor and capacitor tuning ratio, what must be the size and proportions of a single, center-tapped inductance?

We first observe that the total tuning ratio is

$30/3.5 = 8.58$ . If we were to insist on continuous frequency scale coverage of the entire range, ratio  $K_2/K_1$  must be  $(8.58)^{1/2} = 2.93$ . This is dangerously close to 3, so that third harmonic response would be appreciable if this ratio were used. We therefore choose the nearest value of  $K_2/K_1$  that is a preferred operating point, or  $K_2/K_1 = 3.5$ , realizing that in so doing we must allow a gap to exist in the frequency coverage, if we must still tune 3.5-30 Mc. (Continuous coverage with  $K_2/K_1 = 3.5$  requires a capacity tuning ratio of  $(3.5)^2 = 12.25$ , which is impractically high.)

From Fig. 6 at  $K_2/K_1 = 3.5$ , we find  $K_2 = 1.92$ ,  $K_1 = 0.55$  and  $k = 0.3$ . From Fig. 7 at  $k = 0.3$  we find  $l/d$  of the coil to be 1.05. Arbitrarily

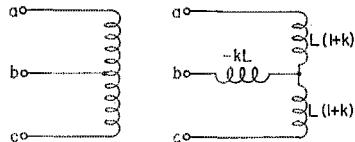


Fig. 7 — T equivalent of a center-tapped coil.

arily setting the lower band limit at 3.4 Mc. to insure coverage at 3.5 Mc., resonant frequency  $f_{01}$  is  $3.4/K_1 = 3.4/0.55 = 6.19$  Mc. With a capacitor tuning ratio of 9:1,  $f_{02} = 3 \times 6.19 = 18.55$  Mc. Thus the two bands are  $6.19 \times 0.55 = 3.4$  Mc. to  $18.55 \times 0.55 = 10.2$  Mc., and

$6.19 \times 1.92 = 11.9$  Mc. to  $18.55 \times 1.92 = 35.6$  Mc. No coverage is obtained between 10.2 Mc. and 11.9 Mc., but this is unimportant for amateur applications.

The design is therefore complete. One selects a coil such that *one half of the coil* has a length-to-diameter ratio of 0.525, and for a given maximum value of capacitor  $C$ , finds the number of turns this half-coil must have to resonate at 6.19 Mc. The final coil has just twice the number of turns and twice the length of the half-coil. The capacitor must be at least 9 times the minimum value

expected, which minimum includes strays and tube capacitances. Thus a capacitor of maximum value about 200  $\mu\text{uf}$ . per section is necessary if a 9:1 capacity tuning ratio is required.

The circuit can be tested by first tuning only half of the coil by  $C$ , with the remainder of the circuit disconnected. A grid-dip meter can be used to indicate resonance in the usual way. Connecting the remainder of the circuit as in Fig. 5, a grid-dip meter coupled to the coil will show the desired resonance points. Depending on coupling to the grid-dip meter, *three* dips may be noted as the grid-dip meter is tuned, for any setting of  $C$ . These will be at a low, medium and high frequency. The one at medium frequency may be disregarded; it is the series-resonant frequency of the circuit. Only the lowest and highest dip need be considered, and these should be close to the calculated values.

#### Experimental Verification

A Barker & Williamson Type 3015 coil (1-inch diameter, 16 turns per inch) was used in a test circuit. The coil used had 34 turns total, and was center-tapped and connected with ganged 150- $\mu\text{uf}$ . capacitors in the circuit of Fig. 5. Resonant frequencies were measured with a grid-dip meter, using the calibration of the meter (which is not highly accurate). The following results were obtained:

	Measured	Calculated
Band A	3.45 — 11.4 Mc.	3.41 — 11.15 Mc.
Band B	10.4 — 35.9 Mc.	10.4 — 34.0 Mc.

#### Summary

This article has given essential design relations for the two-coil and center-tapped single-coil cases of wide-range tuning circuits. Application of these circuits, especially the latter (Fig. 5), to transmitters can result in much more compact equipment than has been possible with band-switching circuits, with resultant saving in cost, complexity and efficiency.

(Continued on page 122)


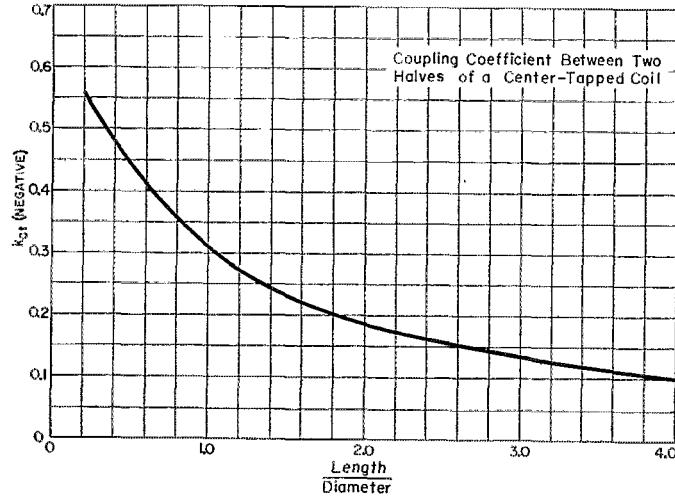


Fig. 8 — Curve of  $k$  vs.  $l/d$  for center-tapped coil.

# LOOK

## Single Sideband

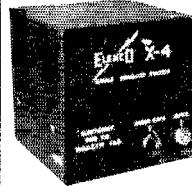

mobile or fixed

### X-4 SSB EXCITER

Only 6" x 6" x 6", 10 watts peak output. Same type crystal filter used in SS-75. Output frequency 3.6 to 4 M.C. Provision for VFO input or crystal operation. Power required: 6.3 V., 1.6 A., 200-300 V.D.C.

80 MA., 45 V. bias. Wired, tested, aligned. **\$49.50**



### ELENCO X-4 VFO

Only 4" x 4" x 2". Modified Clapp circuit, very stable, finest components. Plugs into X-4 Exciter, tunes 3.6 to 4 M.C. Upper or lower sideband selection. Wired, tested. **\$24.50**



### WRIGHT T-R SWITCH

For break-in operation on CW, AM, or SSSC. Use one antenna for transmitting and receiving. It's instantaneous! No moving parts, no power needed to operate. Coax fitting for connections to feeder and receiver. Will handle 1 Kw. With 75 meter plug-in coil. **\$9.95**  
40, 20 meter coils, **\$1.75** each



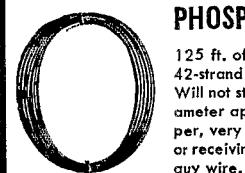
### 8/8/8 MFD. 500 V. D.C.

Triple 8 mfd. 500 working volt D.C. oil-filled condenser, common negative, solder terminals, hermetically sealed, 5" x 3 1/8" x 2 1/4". **\$1.95**



Triple 8 mfd. 450 V. electrolytic upright can condenser, separate negatives, all leads insulated from can. Nationally known mfr. Reg. dealer **59¢**  
net \$2.58. **ONLY 10 for \$5.00**



125 ft. of the finest aerial wire obtainable. 42-strand phosphor-bronze with linen center. Will not stretch, very high tensil strength, diameter approximately same as No. 14 copper, very flexible. Excellent for transmitting or receiving antenna, control cable, guy wire. Regular list \$4.95. **90¢**

**Steinbergs**

Phone CHerry 1880

633 WALNUT STREET • CINCINNATI 2, OHIO

## Multiband Tuning Circuits

(Continued from page 28)

It is also felt that these circuits can be applied to receivers, when it is *desired* to have simultaneous coverage of two bands. Using a harmonic relation (such as 2.0) for ratio  $K_2/K_1$ , one can have r.f. circuits (and hence a receiver) with eventually simultaneous coverage of two bands. Such a receiver has some obvious applications for contest work where one may operate on two bands at once or in close sequence. Tuning rates are in the ratio  $K_2/K_1$  (in this case 2, 3 or 4), so identification of signals as to band is possible.

This article has not been intended to cover other important factors, such as resonant impedance under various coupling situations, bandwidth, loaded  $Q$ , etc. Further experimental work will undoubtedly bring forth improvements and further modifications of the circuit, as well as actual data on factors omitted from this article.

## Never-Never Land

(Continued from page 30)

ably to the mechanical strength of the chassis.

It is easy to get into trouble in the circuit layout if you have one tube performing too many jobs, or if you use regeneration or other shortcuts in the hope of getting good performance with too few tubes. The best way is to use plenty of stages at low gain and separate tubes for each job. The usual precautions about short grid and plate leads have to be taken also, and the old rule about keeping an i.f. amplifier strip (for any one frequency) in a straight line is a good one. If you put the power supply, last audio stage and speaker in a separate cabinet, you will keep your receiver cabinet cool and away from the mechanical vibrations of the speaker.

### Dials

Don't overlook the importance of a good dial mechanism. You can build your own by using one of the popular planetary-drive units and making a dial bezel of thin metal or plastic. A dial scale can be made of cardboard, with dial lights added for a de luxe job. This type of dial allows a half-circle scale length.

If you have some gears from surplus equipment, you can make a dial that will go around about 330 degrees while the condenser rotates 180 degrees. Naturally, such a dial will give nearly twice the scale length of the half circle. An example is shown in Figs. 3 and 6.

Remember to keep the dial simple. A direct-reading single dial is easier to read than a two-dial system or one that requires interpolation. There are many types — slide rule, drum, semi-circle and others — but the one that gives the most dial length in a given space is the circular dial. Above all, the most important thing is to have a dial with plenty of bandspread and no backlash.

(Continued on page 124)